

---

# Lab 2

## MIPS Assembly Programming



Date : 2021.04/09

NAME : 김태윤

Student Number : 2019707033

---

# Contents

## 1. Simulation of MIPS Single Cycle Processor

### A. Result of Simulation

## 2. Simulation of Fibonacci


### A. Result of Simulation

## 3. HOMEWORK; Extend Simple MIPS Single Cycle Processor


### A. Implementing "bne"

# 1. Simulation of MIPS Single Cycle Processor


## A. Result of Simulation

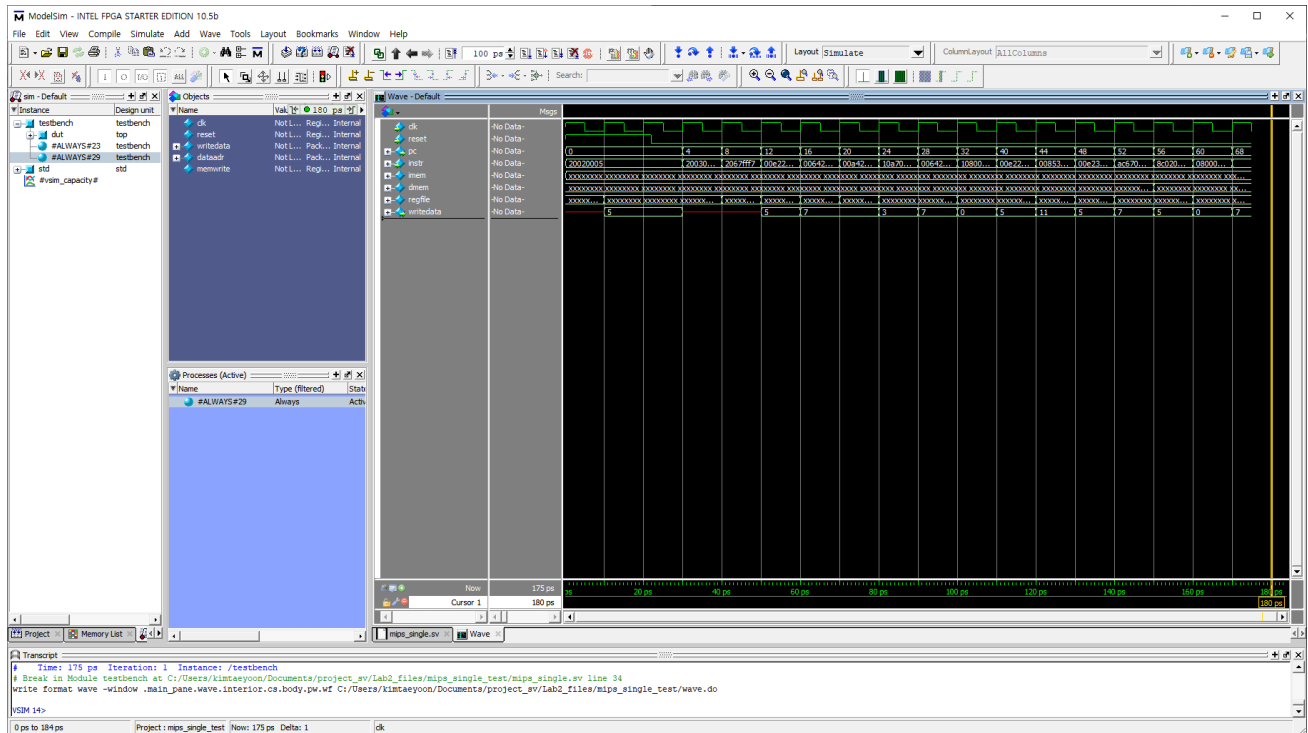

 
Full shot of Simulation layout on my computer.



 We can see program counter was working well like guide.



Also, Register file was working well.

 

Dmem, which have to be 7 to make interrupt to process, was working well too.

## 2. Simulation of Fibonacci

### A. Result of Simulation

- Modification

```
// check results
always @(negedge clk)
begin
    if(memwrite) begin
        if(dataadr == 84 & writedata == 7) begin
            $display("Simulation succeeded");
            $stop;
        end else if (dataadr != 80) begin
            $display("Simulation failed");
            $stop;
        end
    end
end
endmodule
```

->

```
// check results
always @(negedge clk)
begin
    if(memwrite) begin
        if(dataadr == 84 & writedata == 10) begin
            $display("Simulation succeeded");
            $stop;
        end else if (dataadr != 80) begin
            $display("Simulation failed");
            $stop;
        end
    end
end
endmodule
```

```
module imem(input logic [5:0] a,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    initial
        $readmemh("testfile.dat",RAM);

    assign rd = RAM[a]; // word aligned
endmodule
```

->


```
module imem(input logic [5:0] a,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    initial
        $readmemh("fibonacci.dat",RAM);

    assign rd = RAM[a]; // word aligned
endmodule
```

- Simulation

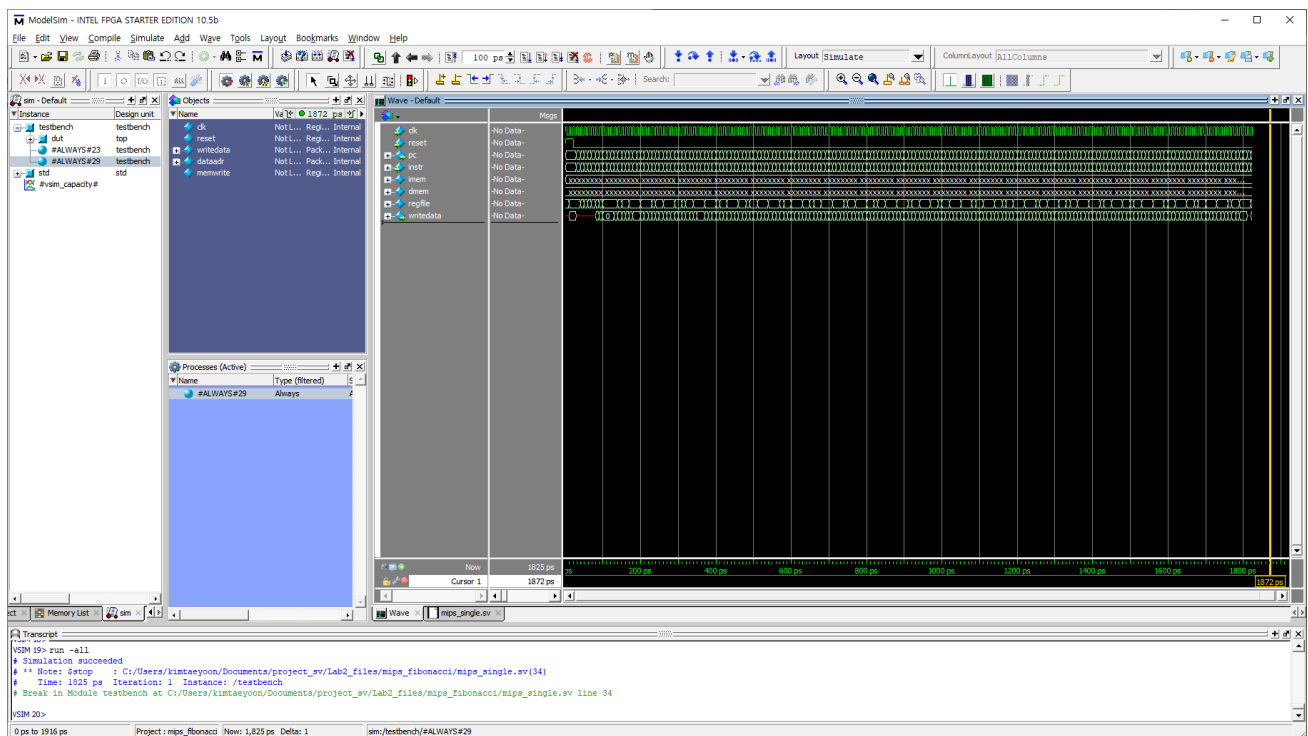

With wave.do, setting up Simulation's environment was very comfort.

```
VSIM 19> run -all
# Simulation succeeded
# ** Note: $stop : C:/Use
# Time: 1825 ps Iteratic
# Break in Module testbench
VSIM 20>
```

[illegible]

+ /testbench/dut/mip...	-No Data-	10946	
+ writedata	-No Data-		10

### 3. HOMEWORK; Extend Simple MIPS Single Cycle Processor

First, we have to know what we have to change for implement "bne". Also, we have to understand how beq, bne works.

In above datapath, it features how beq instruction works. On the top of this datapath, PCSrc(Program Counter source) is generated by Control signal(Branch) and Zero register's & operations's result.

---

1. Show the modifications on the simple MIPS single cycle ("mips\_single.sv") System Verilog code.

```
// mips.sv
// From Section 7.6 of Digital Design & Computer Architecture
// Updated to SystemVerilog 26 July 2011 David_Harris@hmc.edu
// -----
module testbench();

    logic        clk;
    logic        reset;

    logic [31:0] writedata, dataadr;
    logic        memwrite;

    // instantiate device to be tested
    top dut(clk, reset, writedata, dataadr, memwrite);

    // initialize test
    initial
        begin
            reset <= 1; # 22; reset <= 0;
        end

    // generate clock to sequence tests
    always
        begin
            clk <= 1; # 5; clk <= 0; # 5;
        end

    // check results
    always @(negedge clk)
        begin
            if(memwrite) begin
                if(dataadr === 84 & writedata === 10) begin
                    $display("Simulation succeeded");
                    $stop;
                end else if (dataadr !== 80) begin
                    $display("Simulation failed");
                    $stop;
                end
            end
        end
end
```

```

        end
    end
endmodule

// -----
module top(input  logic      clk, reset,
           output logic [31:0] writedata, dataadr,
           output logic      memwrite);

    logic [31:0] pc, instr, readdata;

    // instantiate processor and memories
    mips mips(clk, reset, pc, instr, memwrite, dataadr,
              writedata, readdata);
    imem imem(pc[7:2], instr);
    dmem dmem(clk, memwrite, dataadr, writedata, readdata);
endmodule

// -----
module dmem(input  logic      clk, we,
            input  logic [31:0] a, wd,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

    assign rd = RAM[a[31:2]]; // word aligned

    always_ff @(posedge clk)
        if (we) RAM[a[31:2]] <= wd;
endmodule

// -----
module imem(input  logic [5:0] a,
            output logic [31:0] rd);

    logic [31:0] RAM[63:0];

```

```

initial
    $readmemh("fibonacci_bne.dat",RAM);

    assign rd = RAM[a]; // word aligned
endmodule

// -----
module mips(input  logic      clk, reset,
            output logic [31:0] pc,
            input  logic [31:0] instr,
            output logic      memwrite,
            output logic [31:0] aluout, writedata,
            input  logic [31:0] readdata);

    logic      memtoreg, alusrc, regdst,
               regwrite, jump, pcsrc, zero;
    logic [2:0] alucontrol;

    controller c(instr[31:26], instr[5:0], zero,
                 memtoreg, memwrite, pcsrc,
                 alusrc, regdst, regwrite, jump,
                 alucontrol);
    datapath dp(clk, reset, memtoreg, pcsrc,
                alusrc, regdst, regwrite, jump,
                alucontrol,
                zero, pc, instr,
                aluout, writedata, readdata);
endmodule

// -----
module controller(input  logic [5:0] op, funct,
                 input  logic      zero,
                 output logic      memtoreg, memwrite,
                 output logic      pcsrc, alusrc,
                 output logic      regdst, regwrite,
                 output logic      jump,
                 output logic [2:0] alucontrol);

```



```

logic [1:0] aluop;
logic      branch;

maindec md(op, memtoreg, memwrite, branch,
           alusrc, regdst, regwrite, jump, aluop);
aludec  ad(funct, aluop, alucontrol);

assign pcsrc = op[0] ? (branch & ~zero) : (branch & zero); // ---- (Changed)
           // Beq is already working.
           // BEQ's op is 000100,
           // BNE's op is 000101.
           // As well, maybe we can use difference of lsb.
           // So if lsb is 0, -> for beq
           // And if lsb is 1, -> for bne
endmodule

// -----
module maindec(input  logic [5:0] op,
               output logic      memtoreg, memwrite,
               output logic      branch, alusrc,
               output logic      regdst, regwrite,
               output logic      jump,
               output logic [1:0] aluop);

logic [8:0] controls;

assign {regwrite, regdst, alusrc, branch, memwrite,
       memtoreg, jump, aluop} = controls;

always_comb
case(op)
6'b000000: controls <= 9'b110000010; // RTYPE
6'b100011: controls <= 9'b101001000; // LW
6'b101011: controls <= 9'b001010000; // SW
6'b000100: controls <= 9'b000100001; // BEQ
6'b000101: controls <= 9'b000100001; // BNE ---- (Changed)
6'b001000: controls <= 9'b101000000; // ADDI
6'b000010: controls <= 9'b000000100; // J
default:   controls <= 9'bxxxxxxxxx; // illegal op

```

```

        endcase
    endmodule

// -----
module aludec(input  logic [5:0] funct,
              input  logic [1:0] aluop,
              output logic [2:0] alucontrol);

    always_comb
    case(aluop)
        2'b00: alucontrol <= 3'b010; // add (for lw/sw/addi)
        2'b01: alucontrol <= 3'b110; // sub (for beq)
        default: case(funct) // R-type instructions
            6'b100000: alucontrol <= 3'b010; // add
            6'b100010: alucontrol <= 3'b110; // sub
            6'b100100: alucontrol <= 3'b000; // and
            6'b100101: alucontrol <= 3'b001; // or
            6'b101010: alucontrol <= 3'b111; // slt
            default: alucontrol <= 3'bxxx; // ???
        endcase
    endcase
endmodule

// -----
module datapath(input  logic      clk, reset,
               input  logic      memtoreg, pcsrc,
               input  logic      alusrc, regdst,
               input  logic      regwrite, jump,
               input  logic [2:0] alucontrol,
               output logic      zero,
               output logic [31:0] pc,
               input  logic [31:0] instr,
               output logic [31:0] aluout, writedata,
               input  logic [31:0] readdata);

    logic [4:0] writereg;
    logic [31:0] pcnext, pcnextbr, pcplus4, pcbranch;
    logic [31:0] signimm, signimmsh;

```

```

logic [31:0] srca, srcb;
logic [31:0] result;

// next PC logic
flopr #(32) pcreg(clk, reset, pcnext, pc);
adder      pcadd1(pc, 32'b100, pcplus4);
sl2        immsh(signimm, signimmsh);
adder      pcadd2(pcplus4, signimmsh, pcbranch);
mux2 #(32) pcbrmux(pcplus4, pcbranch, pcsrc, pcnextbr);
mux2 #(32) pcmux(pcnextbr, {pcplus4[31:28],
                           instr[25:0], 2'b00}, jump, pcnext);

// register file logic
regfile    rf(clk, regwrite, instr[25:21], instr[20:16],
              writereg, result, srca, writedata);
mux2 #(5)   wrmux(instr[20:16], instr[15:11],
                  regdst, writereg);
mux2 #(32)  resmux(aluout, readdata, memtoreg, result);
signext     se(instr[15:0], signimm);

// ALU logic
mux2 #(32)  srcbmux(writedata, signimm, alusrc, srcb);
alu         alu(srca, srcb, alucontrol, aluout, zero);
endmodule

```

```

// -----
module regfile(input  logic      clk,
               input  logic      we3,
               input  logic [4:0] ra1, ra2, wa3,
               input  logic [31:0] wd3,
               output logic [31:0] rd1, rd2);

logic [31:0] rf[31:0];

// three ported register file
// read two ports combinationaly
// write third port on rising edge of clk
// register 0 hardwired to 0
// note: for pipelined processor, write third port

```

```

// on falling edge of clk

always_ff @(posedge clk)
    if (we3) rf[wa3] <= wd3;

assign rd1 = (ra1 != 0) ? rf[ra1] : 0;
assign rd2 = (ra2 != 0) ? rf[ra2] : 0;
endmodule

// -----
module adder(input  logic [31:0] a, b,
             output logic [31:0] y);

    assign y = a + b;
endmodule

// -----
module sl2(input  logic [31:0] a,
           output logic [31:0] y);

    // shift left by 2
    assign y = {a[29:0], 2'b00};
endmodule

// -----
module signext(input  logic [15:0] a,
               output logic [31:0] y);

    assign y = {{16{a[15]}}, a};
endmodule

// -----
module flopr #(parameter WIDTH = 8)
    (input  logic          clk, reset,
     input  logic [WIDTH-1:0] d,
     output logic [WIDTH-1:0] q);

```

```

always_ff @(posedge clk, posedge reset)
    if (reset) q <= 0;
    else      q <= d;
endmodule

// -----
module mux2 #(parameter WIDTH = 8)
    (input  logic [WIDTH-1:0] d0, d1,
     input  logic             s,
     output logic [WIDTH-1:0] y);

    assign y = s ? d1 : d0;
endmodule

// -----
module alu(input  logic [31:0] a, b,
           input  logic [2:0]  alucontrol,
           output logic [31:0] result,
           output logic        zero);

    logic [31:0] condinvb, sum;

    assign condinvb = alucontrol[2] ? ~b : b;
    assign sum = a + condinvb + alucontrol[2];

    always_comb
        case (alucontrol[1:0])
            2'b00: result = a & b;
            2'b01: result = a | b;
            2'b10: result = sum;
            2'b11: result = sum[31];
        endcase

    assign zero = (result == 32'b0);
endmodule

```

2. Indicate the changed that you made to implement the new instruction.

```
module maindec(input logic [5:0] op,
               output logic memtoreg, memwrite,
               output logic branch, alusrc,
               output logic regdst, regwrite,
               output logic jump,
               output logic [1:0] aluop);

    logic [8:0] controls;

    assign {regwrite, regdst, alusrc, branch, memwrite,
           memtoreg, jump, aluop} = controls;

    always_comb
    case (op)
        6'b000000: controls <= 9'b110000010; // RTYPE
        6'b100011: controls <= 9'b101001000; // LW
        6'b101011: controls <= 9'b001010000; // SW
        6'b000100: controls <= 9'b000100001; // BEQ
        6'b000101: controls <= 9'b000100001; // BNE ---- (Changed)
        6'b001000: controls <= 9'b101000000; // ADDI
        6'b000010: controls <= 9'b000000100; // J
        default: controls <= 9'bxxxxxxxx; // illegal op
    endcase
endmodule
```

I added "6'b000101: controls <= 9'b000100001. It means when opcode is 000101, push 000100001 to control signal so bne works well.

```
module controller(input logic [5:0] op, funct,
                  input logic zero,
                  output logic memtoreg, memwrite,
                  output logic pcsrc, alusrc,
                  output logic regdst, regwrite,
                  output logic jump,
                  output logic [2:0] alucontrol);


    logic [1:0] aluop;
    logic branch;

    maindec md(op, memtoreg, memwrite, branch,
               alusrc, regdst, regwrite, jump, aluop);
    aludec ad(funct, aluop, alucontrol);

    assign pcsrc = op[0] ? (branch & ~zero) : (branch & zero); // ---- (Changed)
    // Beq is already working.
    // BEQ's op is 000100,
    // BNE's op is 000101.
    // As well, maybe we can use difference of lsb.
    // So if lsb is 0, -> for beq
    // And if lsb is 1, -> for bne
endmodule
```

BEQ's opcode is 000100. BNE's opcode is 000101. Just lsb is different. So I think that using ternary operation is the best way. When op[0](LSB) is 1, pcsrc goes branch & ~zero, and op[0](LSB) is 0, pcsrc goes branch & zero. It works well.

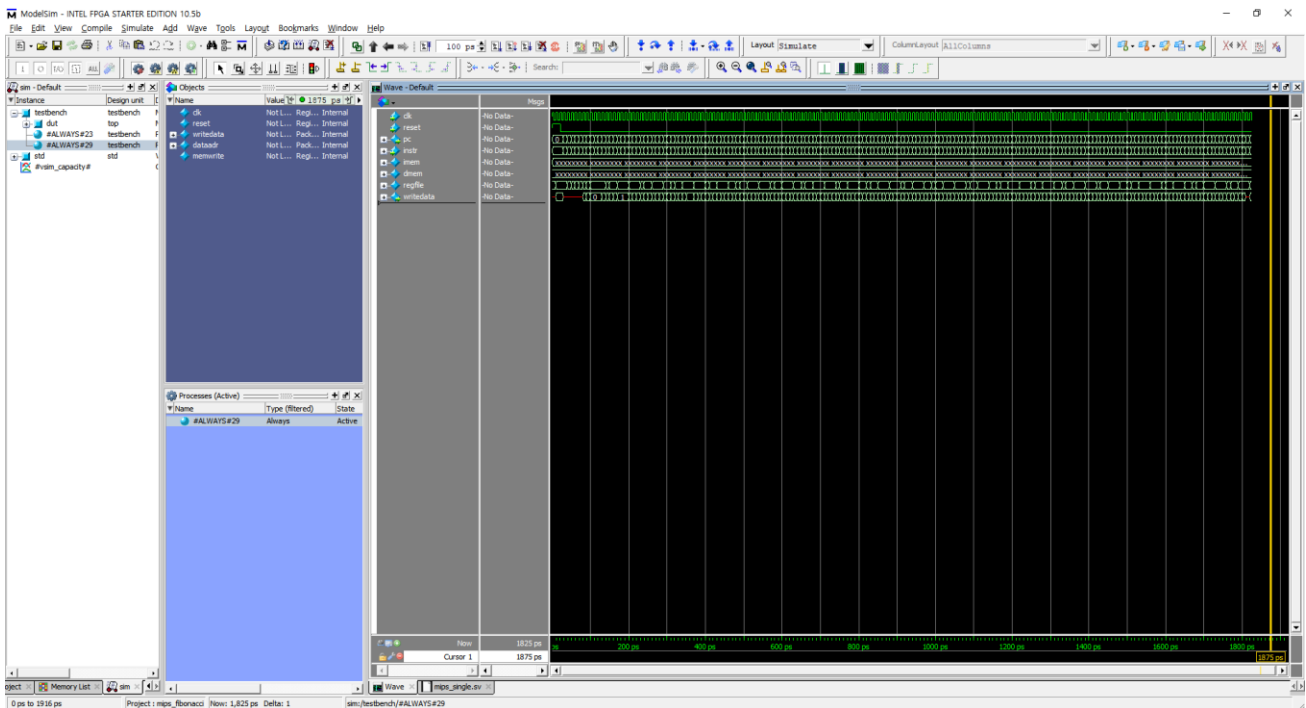3. Show the output wave simulation that contains f[21]=10946 in register \$12 and the value 10 in writedata variable.



Full of my Simulation layout(Fibonacci\_bne)

```
VSIM 31> run -all
# Simulation succeeded
# ** Note: $stop : C:/Use
# Time: 1825 ps Iteratic
# Break in Module testbench
```

[15]	-No Data-	00000001							
[14]	-No Data-	00000001	00000000	00000001	00000000	00000001	00000000		
[13]	-No Data-	987	1597	2584	4181	6765	10946		
[12]	-No Data-	00000262	0000063d		00001055		00002ac2		
[11]	-No Data-	000003db		00000a18		00001a6d			
[10]	-No Data-								
[9]	-No Data-								

We can see ..., {1597, 2584, 4181, 6765, 10946}. It seems works very well.

instr	-No Data-	150d...	21290001	150dffa	1109000b	2002000a	ac020054
imem	-No Data-	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx
dmem	-No Data-	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx
regfile	-No Data-	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx	xxxxxxxx
writedata	-No Data-	0	19	0	20		10

We can see writedata's last value is 10, so simulation terminated successfully.